


Basic/Pipelined processor Implementation

Jinyang Li

Today's lesson plan


- Basic single-cycle CPU design, continued
- Pipelining idea and challenges

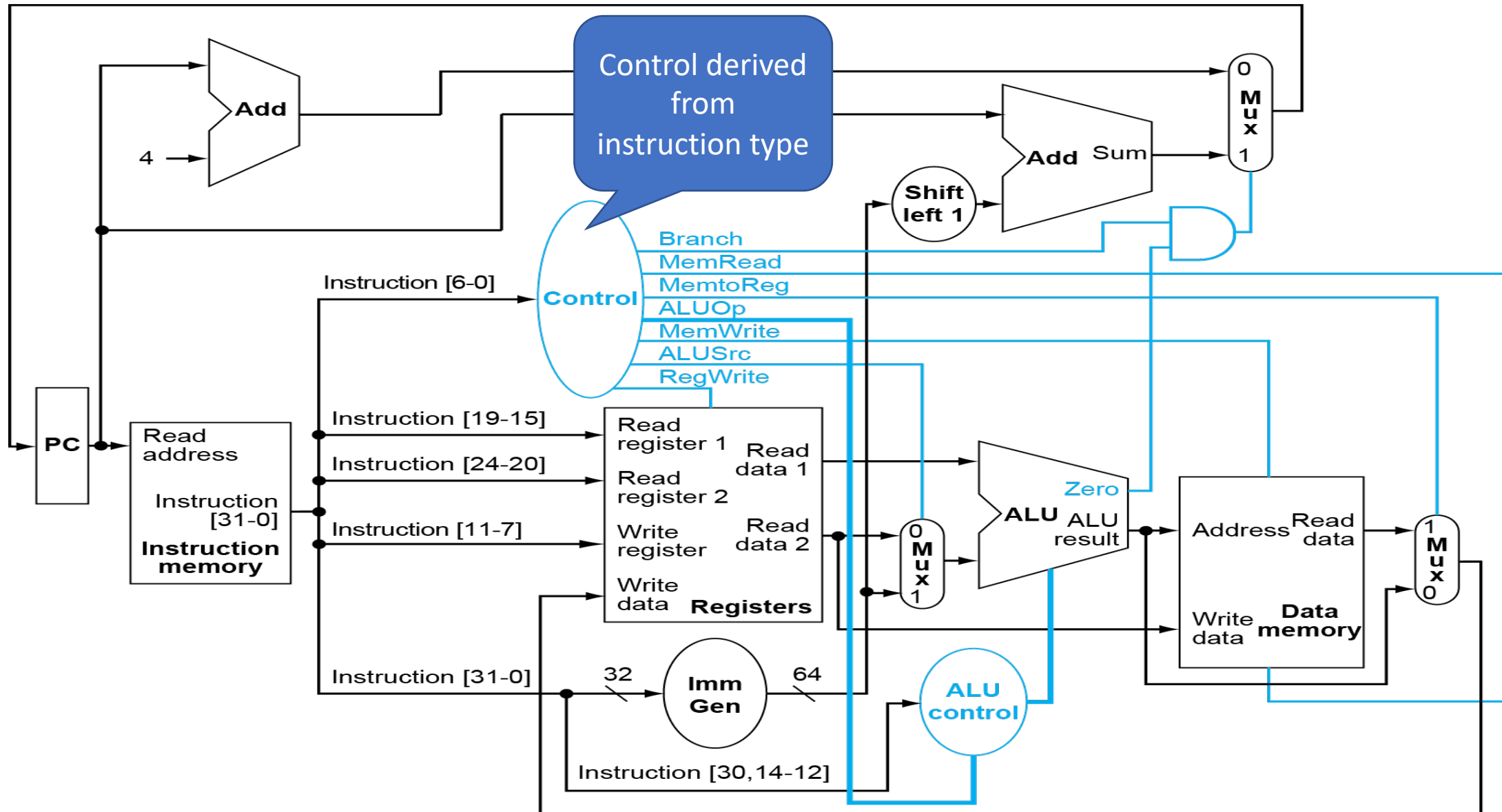Recall our basic RISC-V CPU: datapath w/ control




add x5, x6, x7

R-Type Inst

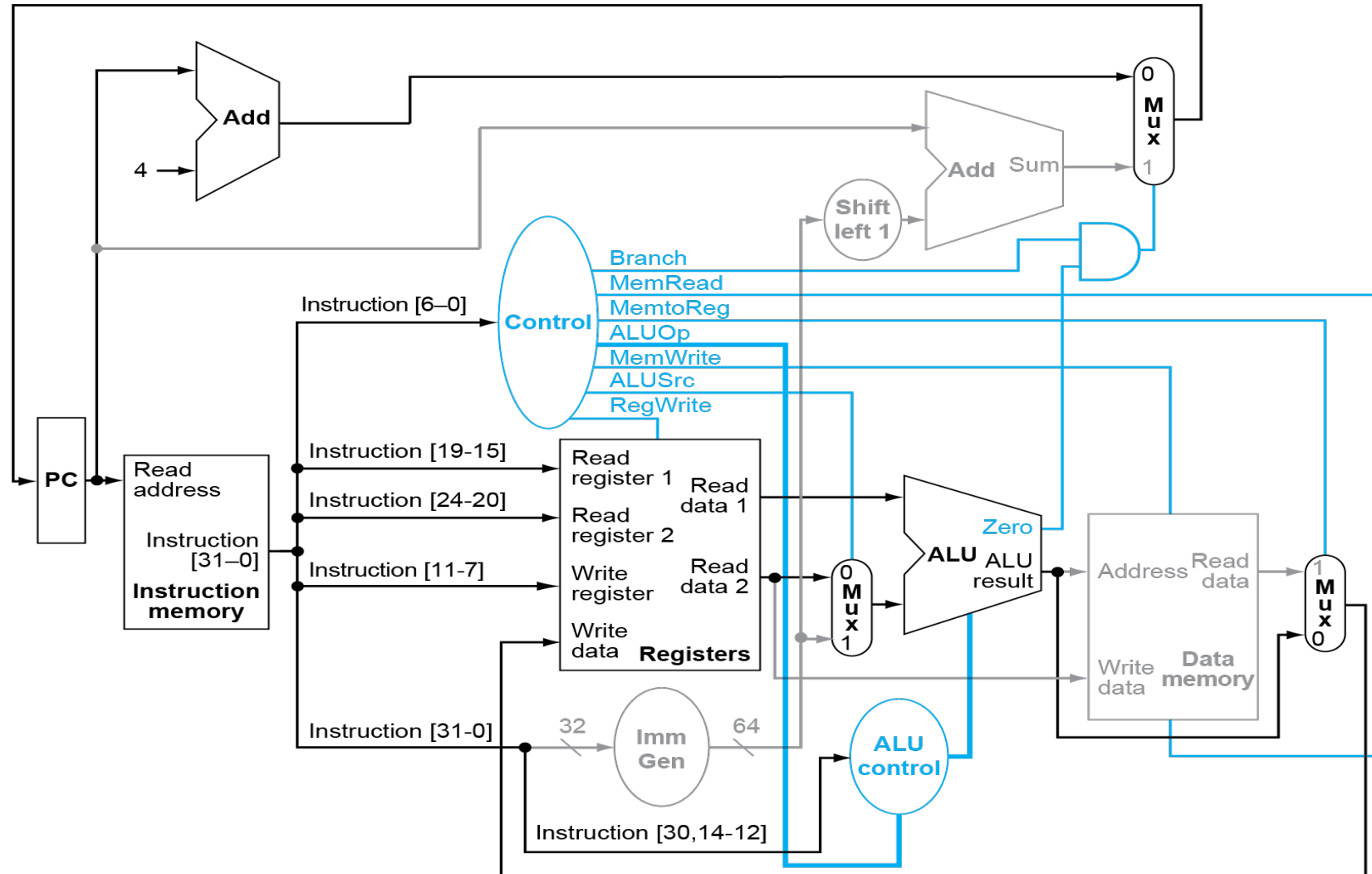

BEQ Instruction


beq x5, x6, 100

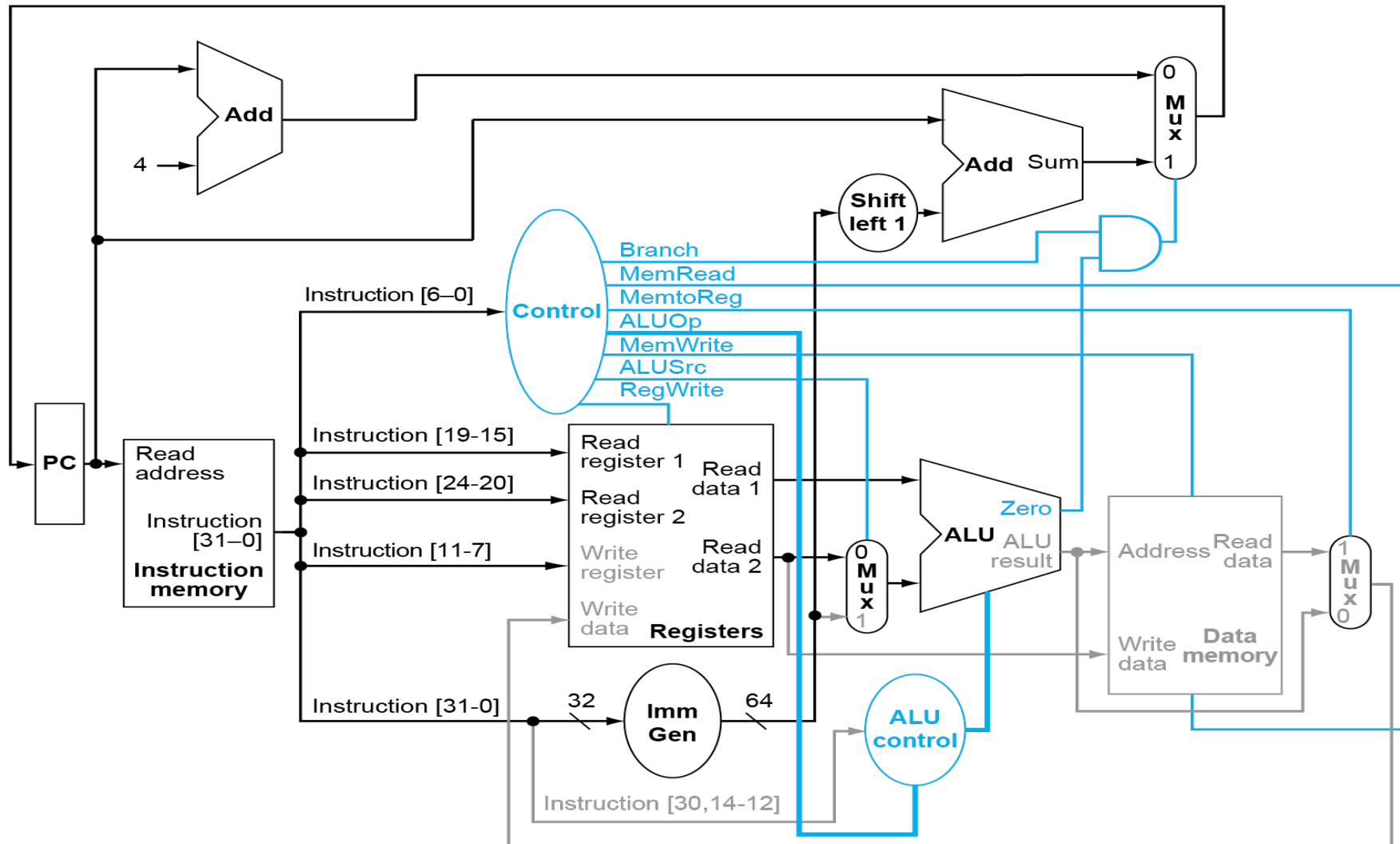


ld x5, 40(x6)

Load Inst

immediate	rs1	funct3	rd	opcode
-----------	-----	--------	----	--------

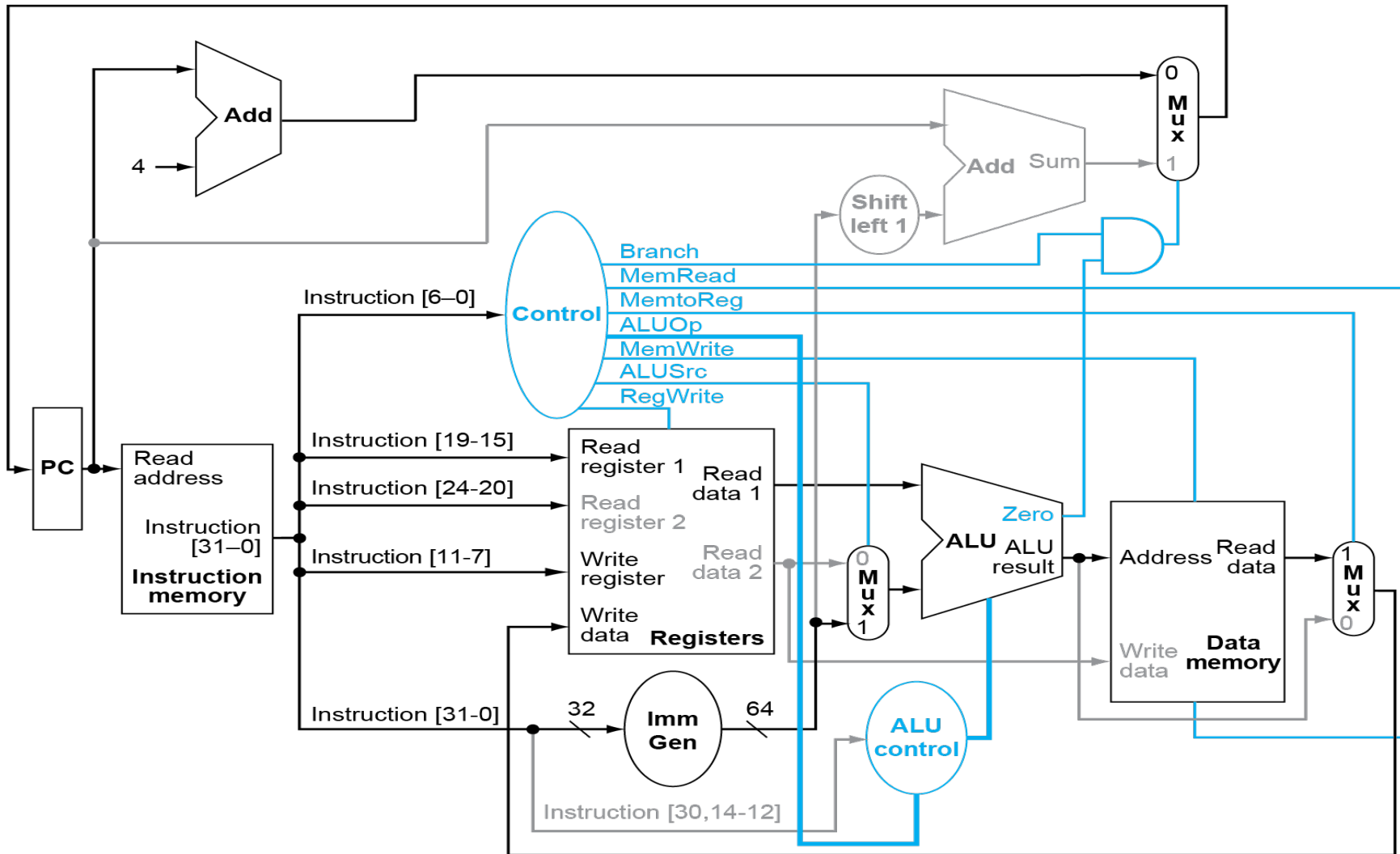

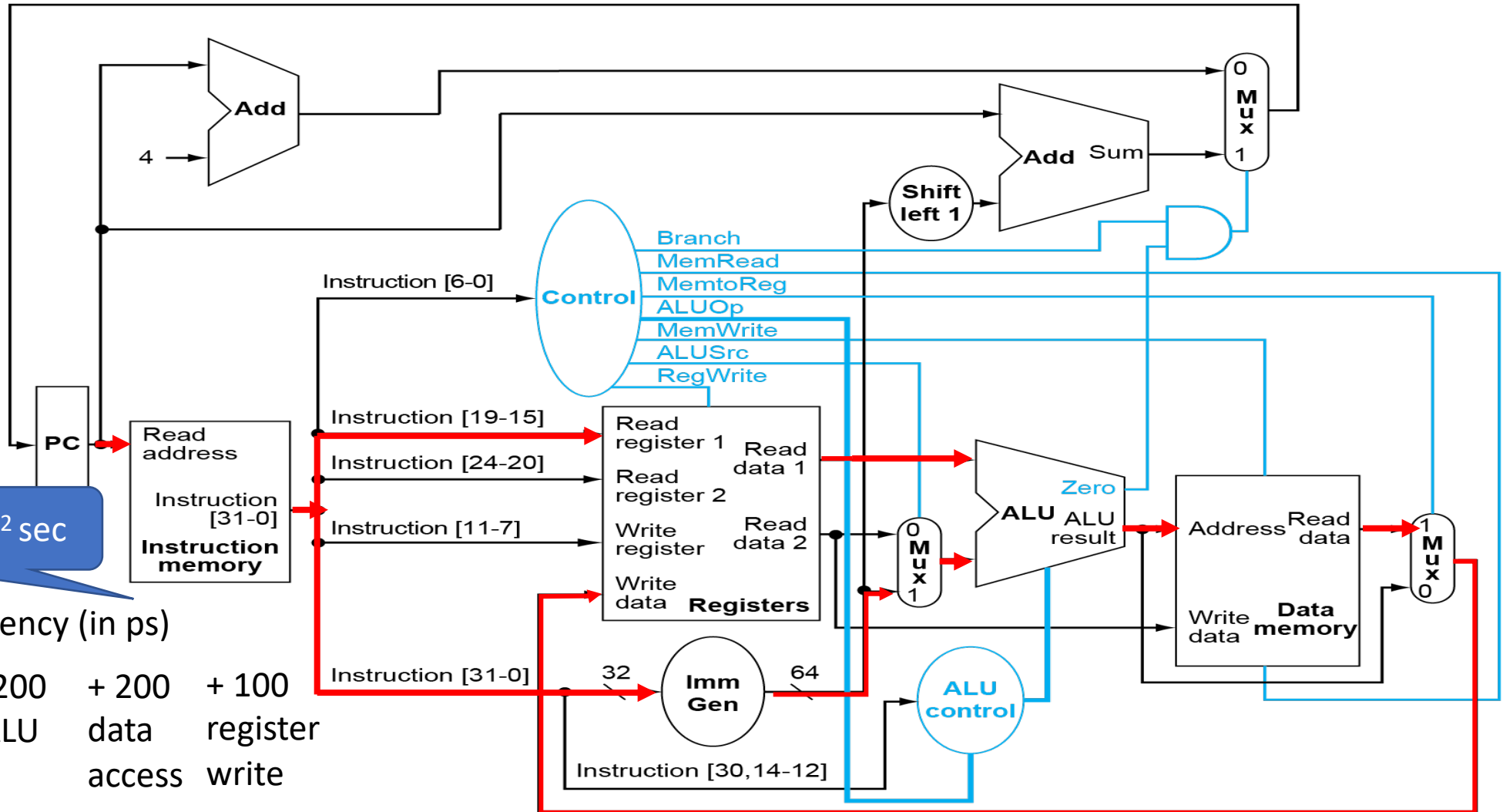Basic CPU must finish an instruction in one clock cycle → use a “slow” clock



1 picosecond = 10^{-12} sec

Load instruction latency (in ps)



200	+ 100	+ 200	+ 200	+ 100
instruction fetch	register read	ALU access	data access	register write

Clock cycle \geq 800 ps

Our basic design is slow

- Longest delay determines clock period
 - Critical path: load instruction
 - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary clock period for different instructions
- Next: improve performance by pipelining

Pipelining: a laundry analogy

  

Pipelined laundry: overlapping execution


- Parallelism improves performance

RISC-V Pipeline


- Five stages:
 1. IF: Instruction fetch from memory
 2. ID: Instruction decode & register read
 3. EX: Execute operation or calculate address
 4. MEM: Access memory operand
 5. WB: Write result back to register

Pipeline Performance

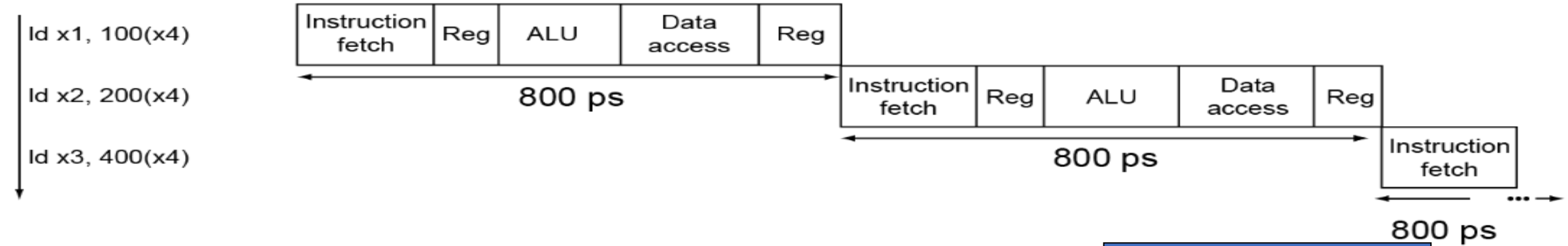Program execution order (in instructions)




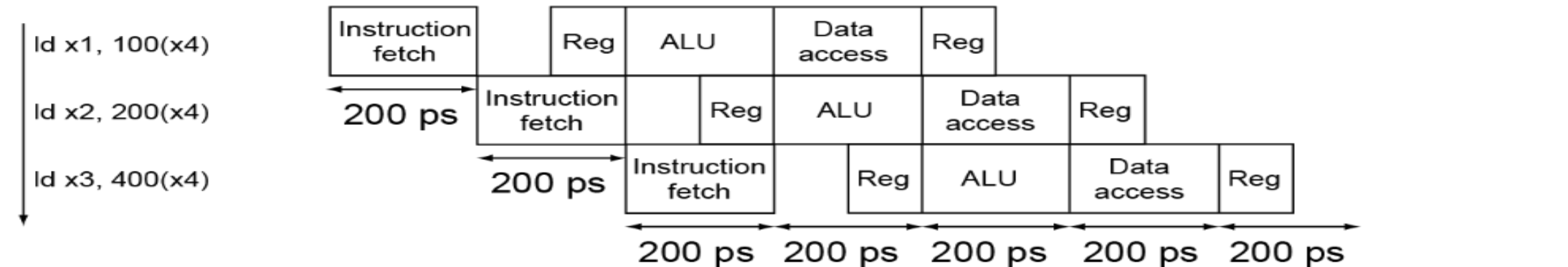Program execution order (in instructions)



Pipeline Speedup

 - Pipelining increases throughput (instructions/sec)
 - Latency (time for each instruction) does not decrease
- If all stages are balanced (i.e., all take the same time)
 - $\text{throughput}_{\text{pipelined}} = \text{number-of-stages} * \text{throughput}_{\text{nonpipelined}}$
 - If not balanced, speedup is less



Throughput = $1/(\text{time between instructions})$

Pipelining and ISA Design

- RISC-V ISA is designed for pipelining
 - All instructions are 32-bits
 - Easier to fetch and decode in one cycle
 - c.f. x86: 1- to 17-byte instructions
 - Few and regular instruction formats
 - Can decode and read registers in one step
 - Load/store addressing
 - Can calculate address in 3rd stage, access memory in 4th stage

Pipeline challenges: hazards


- Situations that prevent starting next instruction in the next cycle
- Structure hazard
 - A required resource is busy
- Data hazard
 - Need to wait for previous instruction to complete its write
- Control hazard
 - Which instruction to execute depends on previous instruction

Structure Hazards

- Conflict use of a single resource
- Example: Suppose CPU uses a single memory
 - Load/store requires data access
 - Instruction fetch would have to *stall* for that cycle
 - Would cause a pipeline “bubble”
- Solution: Use separate instruction/data memories

Data Hazards

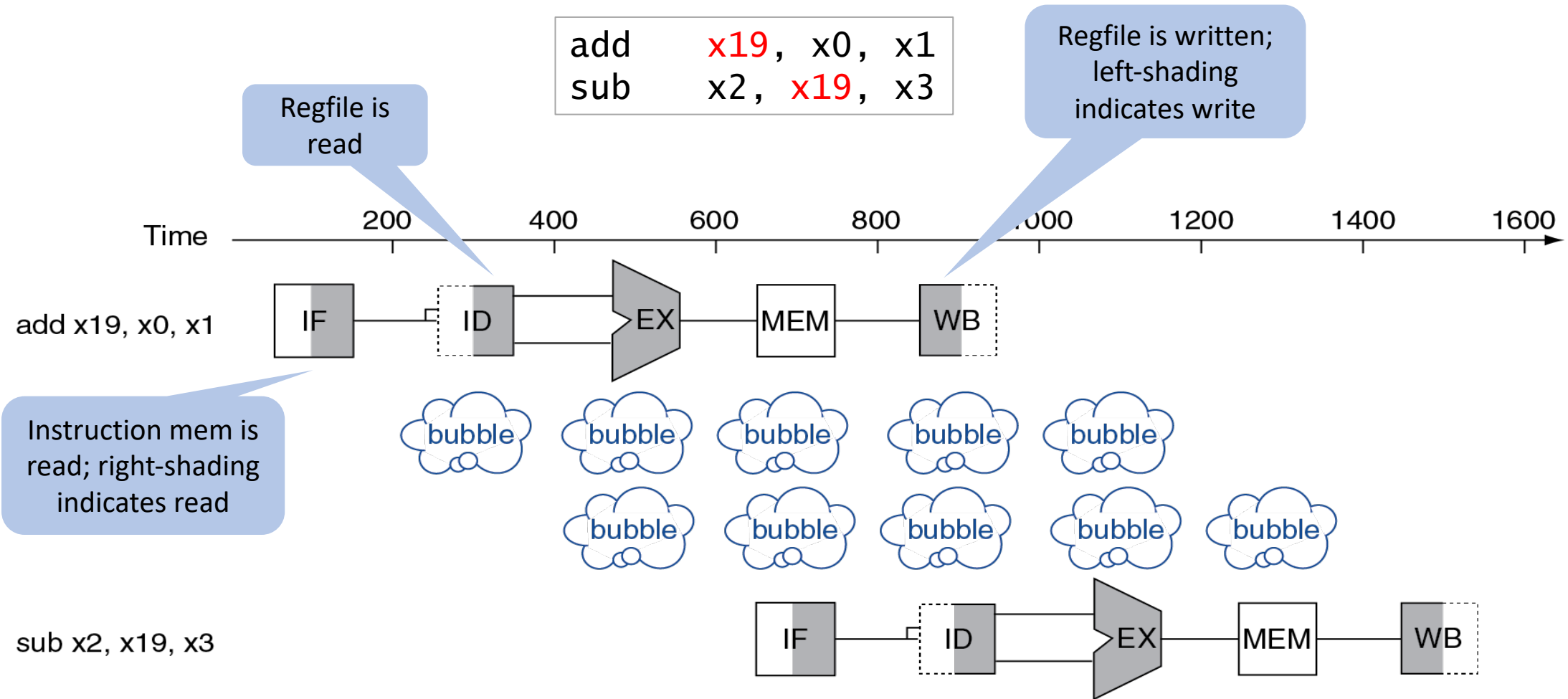- An instruction depends on the previous instruction to complete its write




Control hazard

- Wait until branch outcome is determined before fetching next instruction


Program execution order (in instructions)

add x4, x5, x6
beq x1, x0, 40

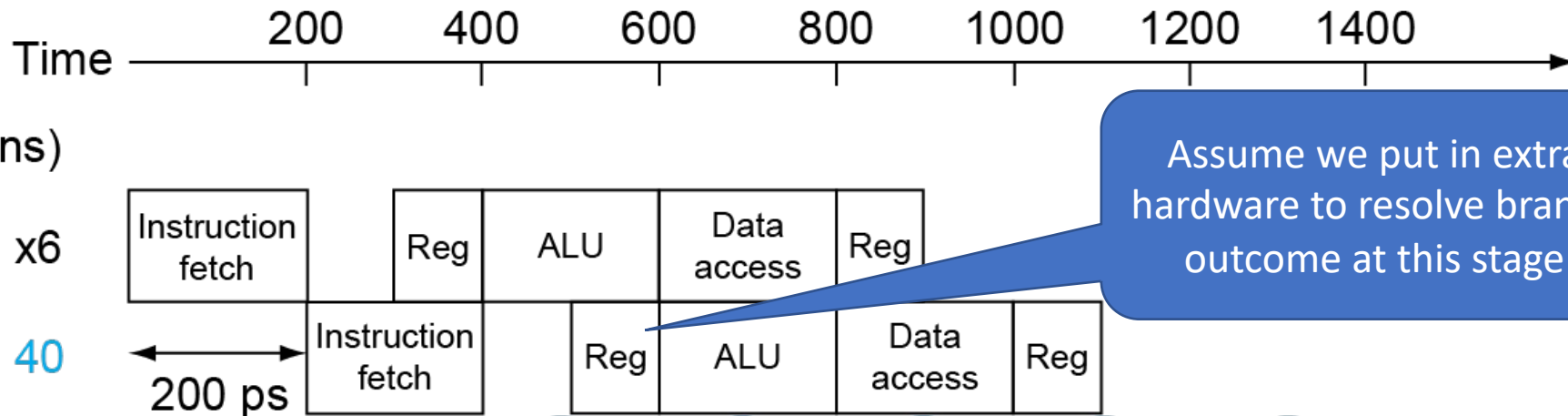


Control hazard

 - Wait until branch outcome is determined before fetching next instruction



A basic pipelined RISC-V CPU


Pipelined Datapath

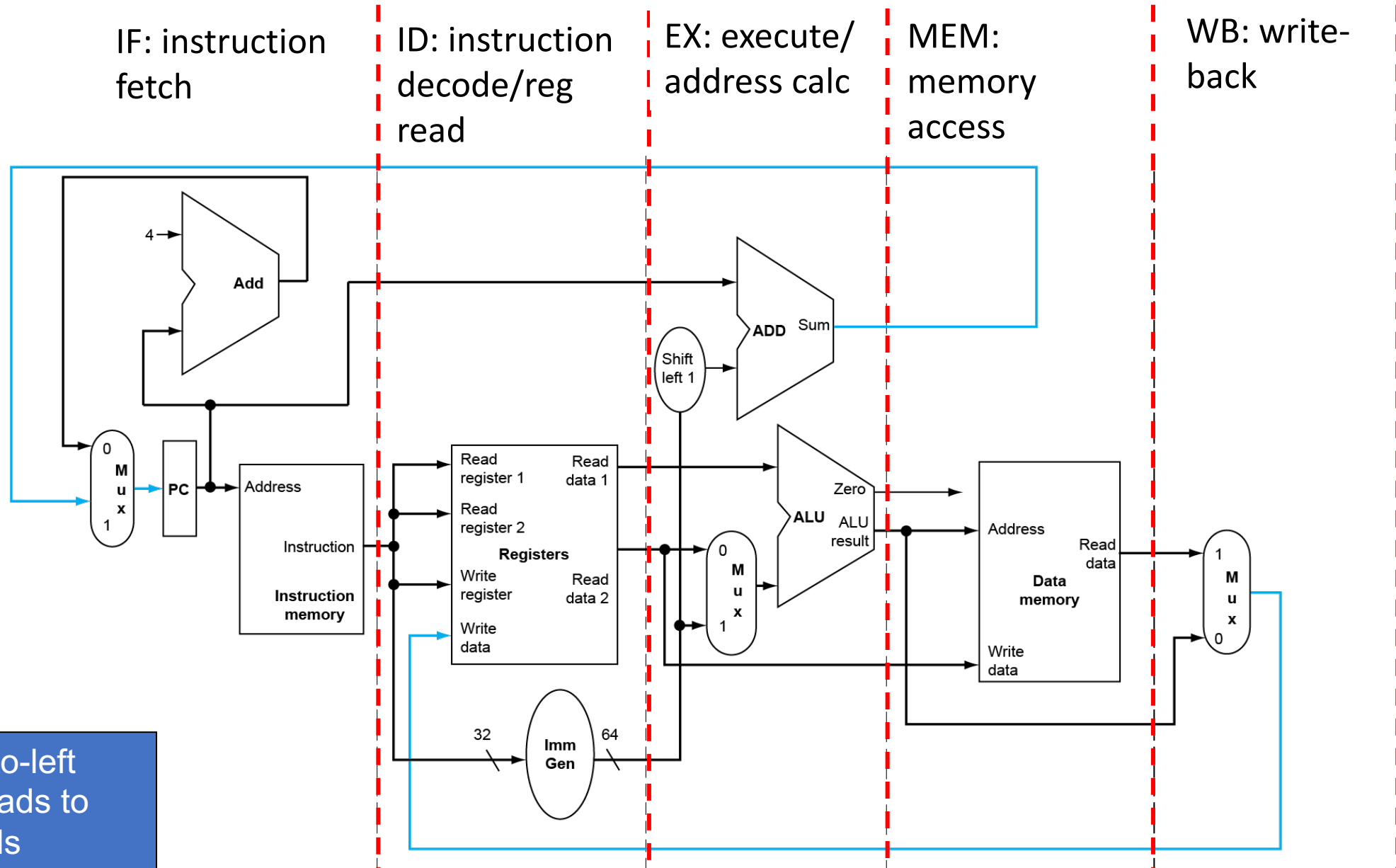


Right-to-left flow leads to hazards

Pipeline registers

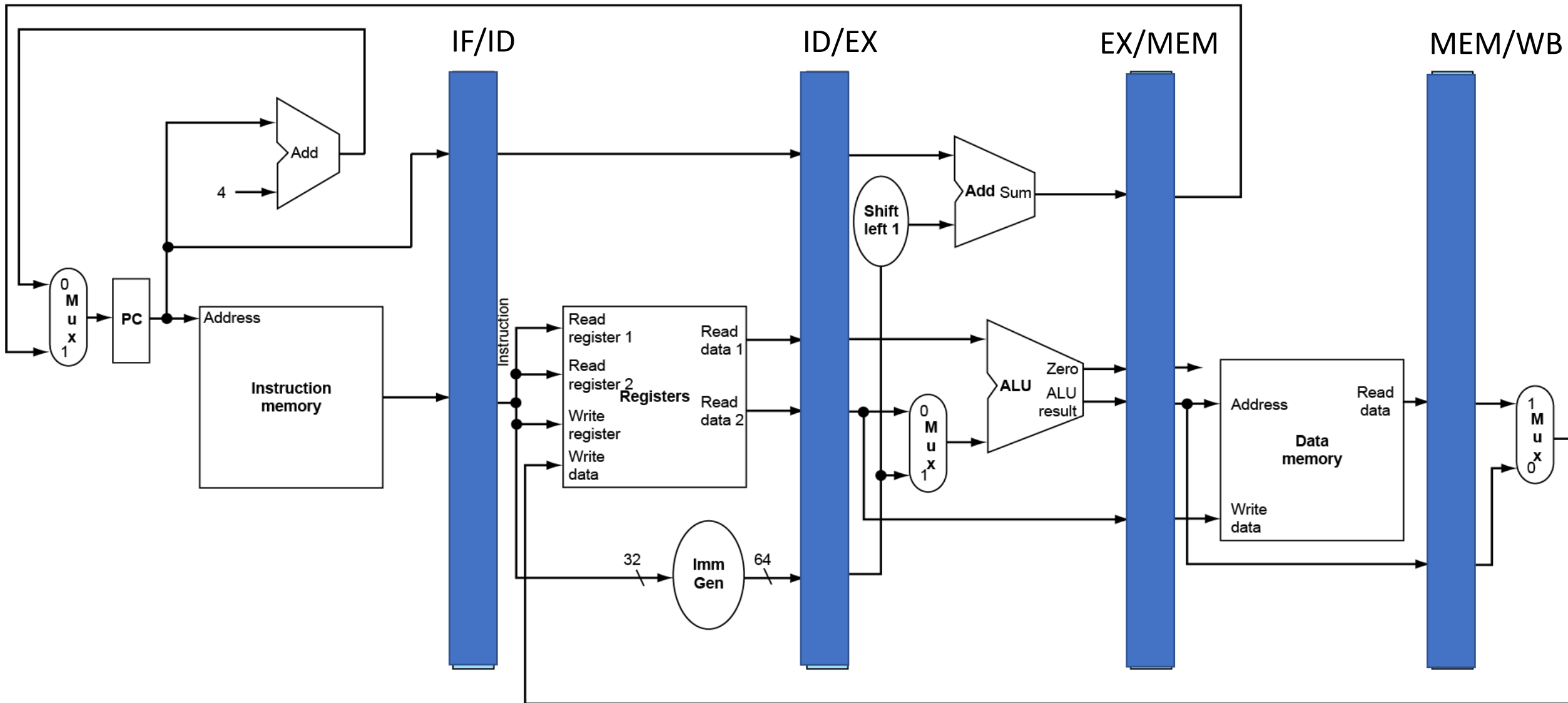
: needed to hold data produced in previous cycle





IF for Load, Store

 

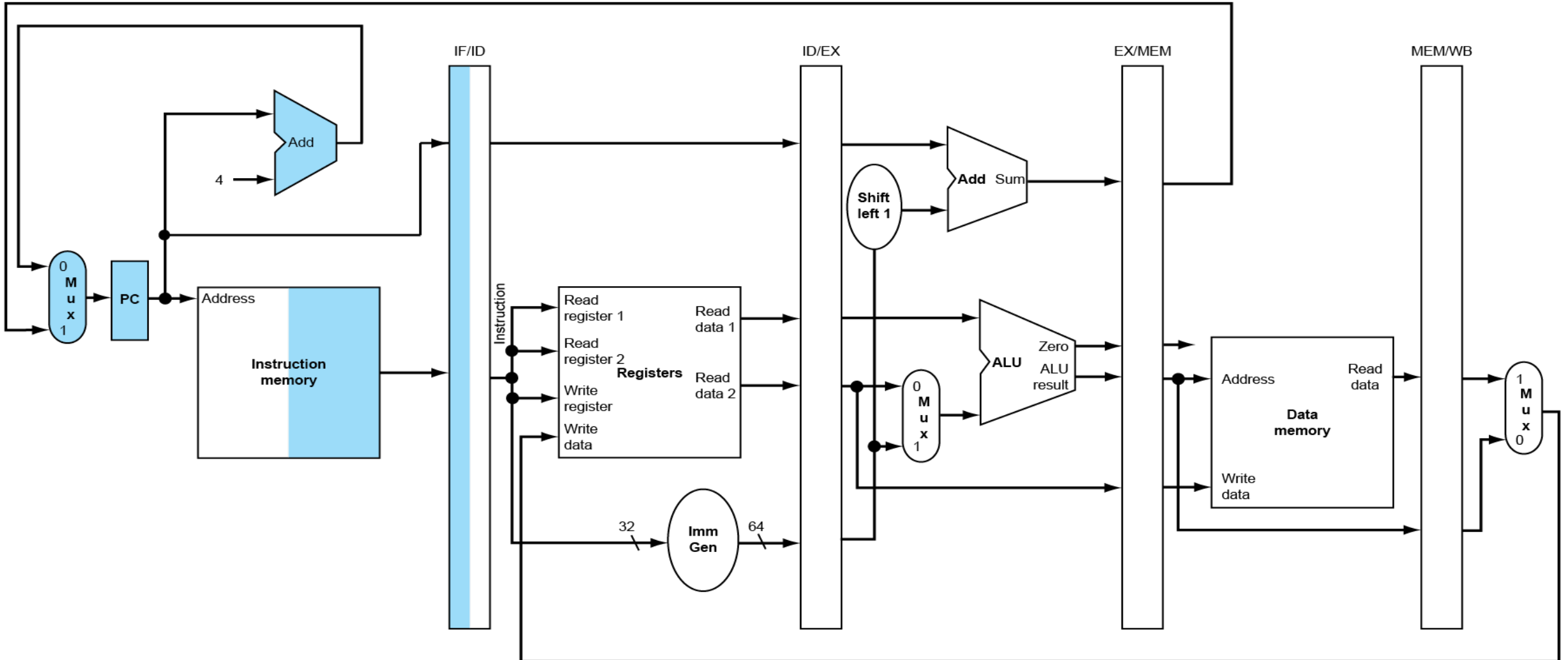
Single-clock-cycle diagram shows the state of an entire datapath during a single clock cycle




ID for Load, Store, ...

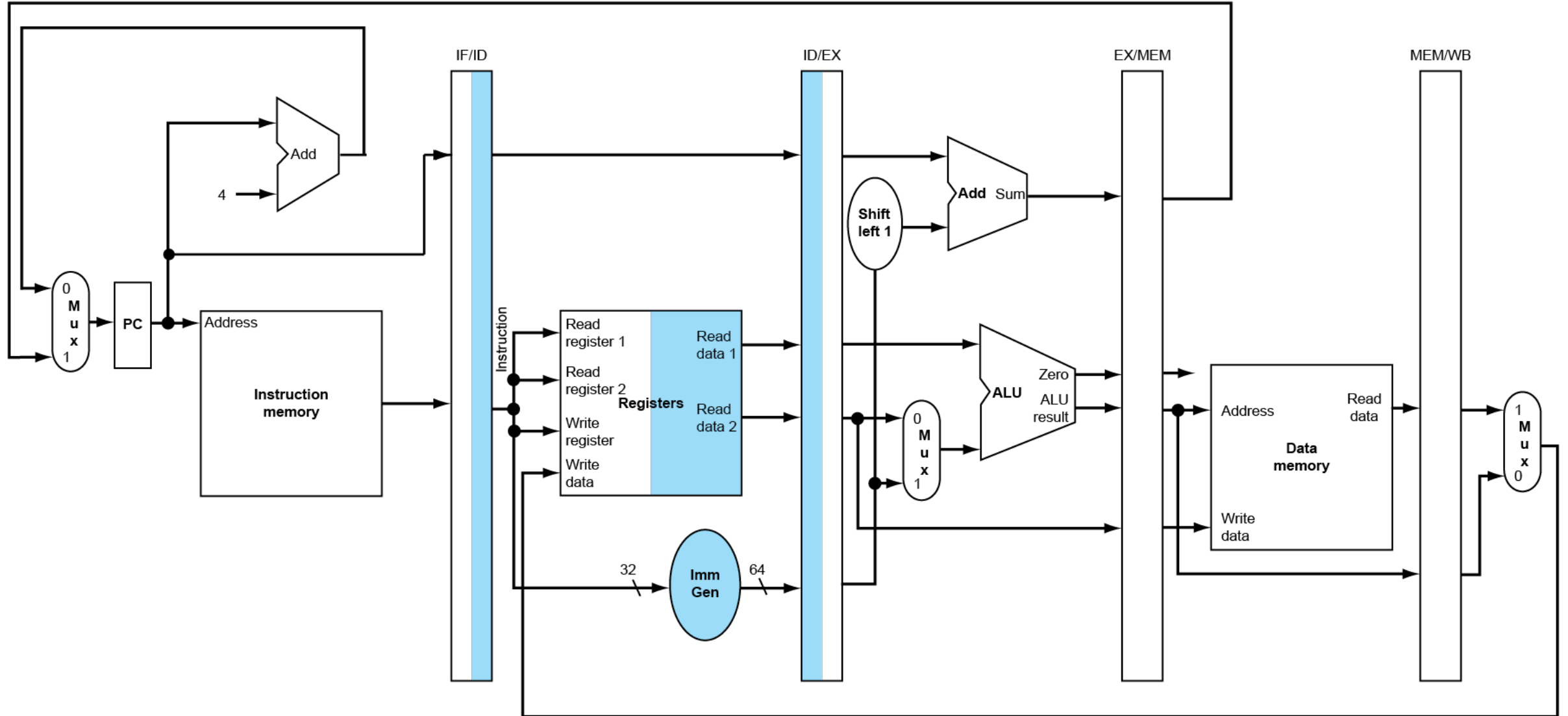 

EX for Load

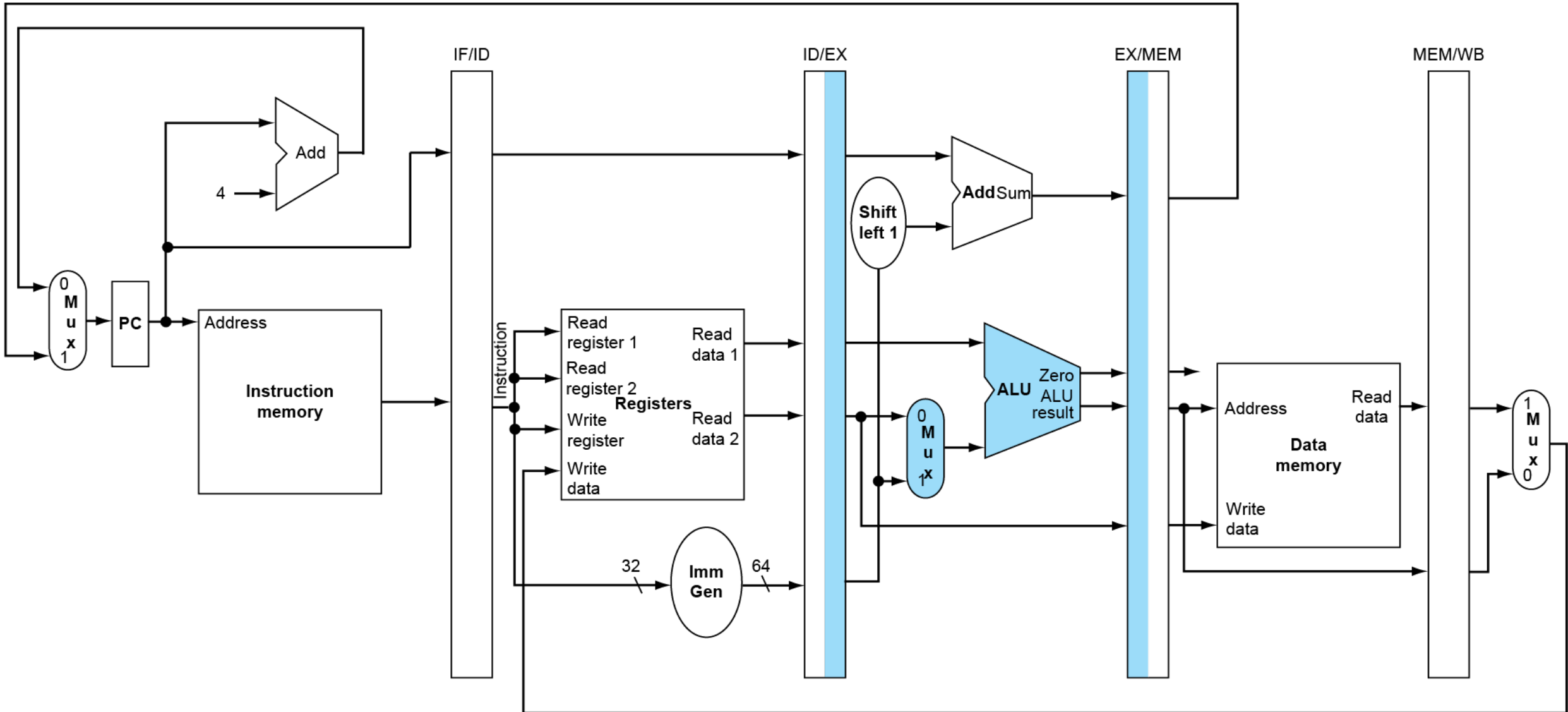


MEM for Load

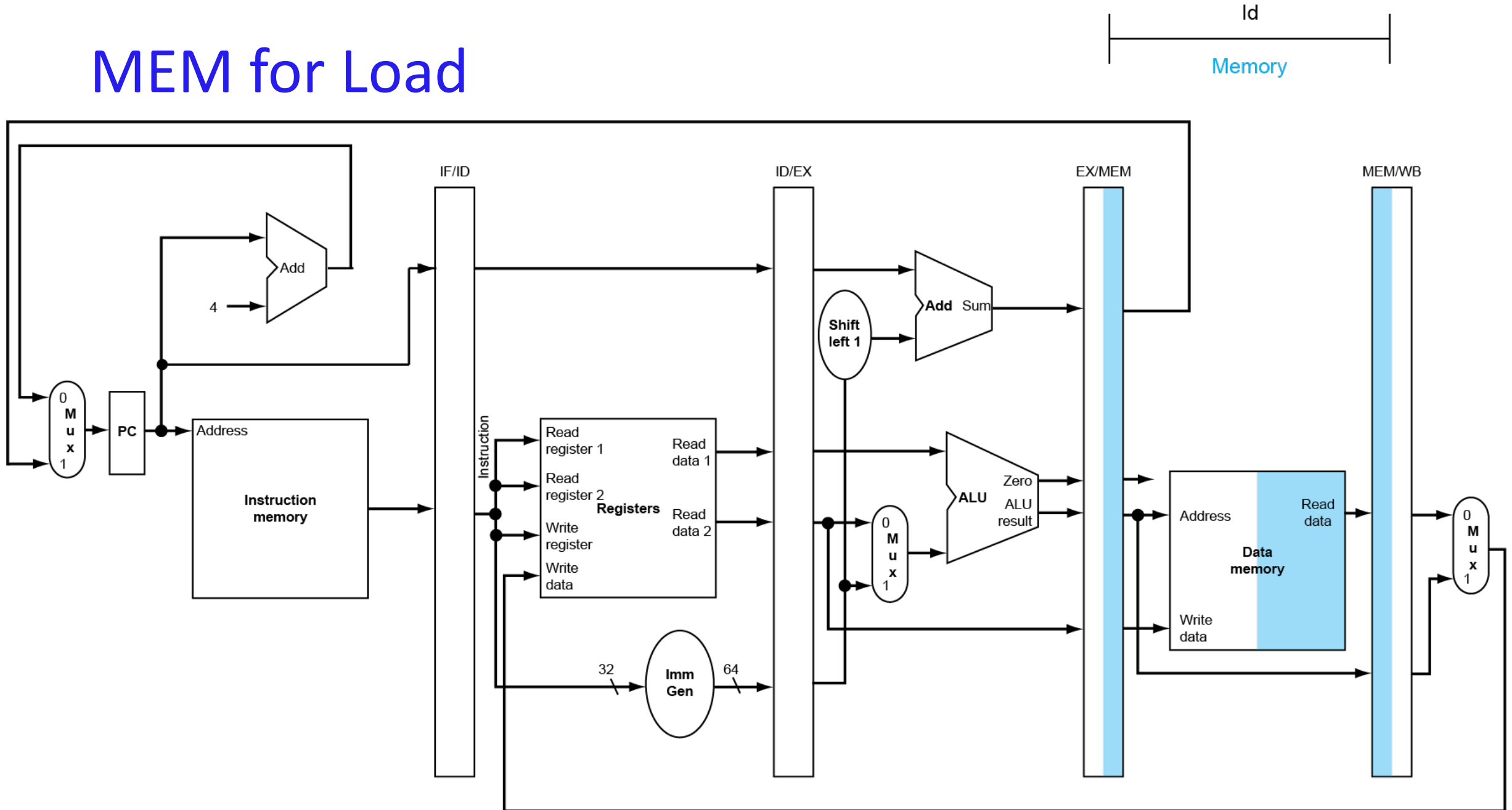


WB for Load



ld
Write-back

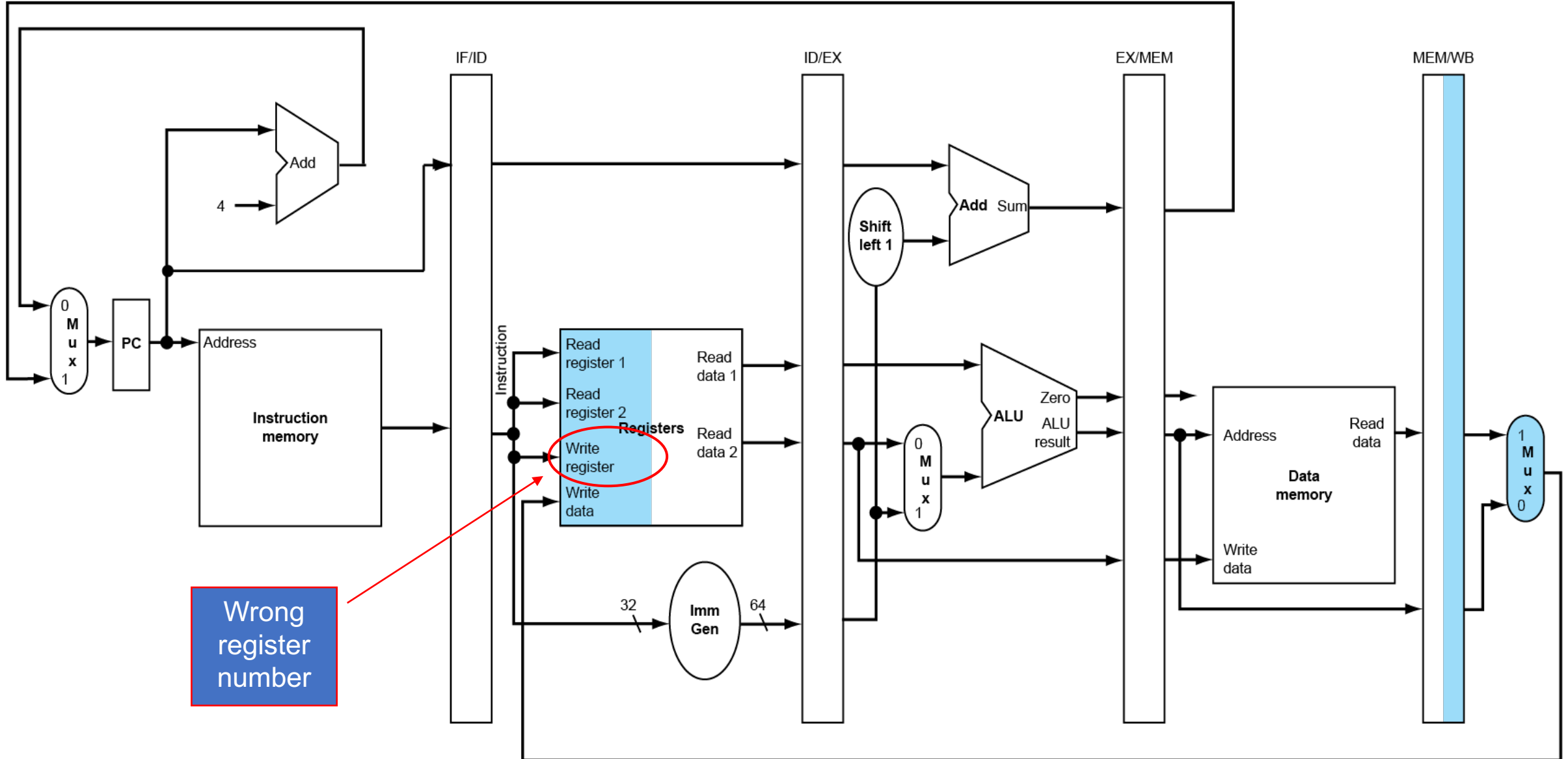


Corrected Datapath for Load

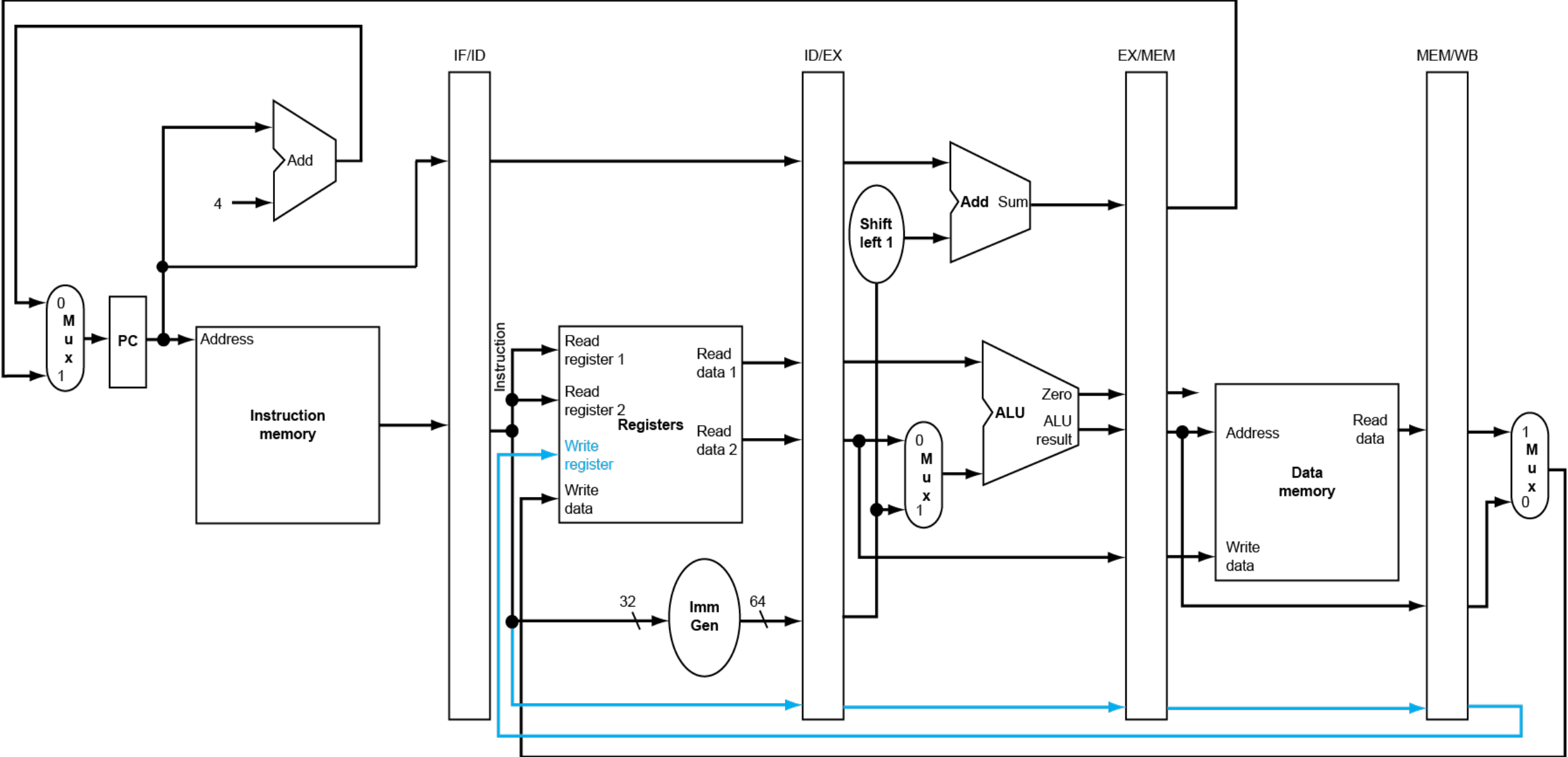

EX for Store

  


MEM for Store

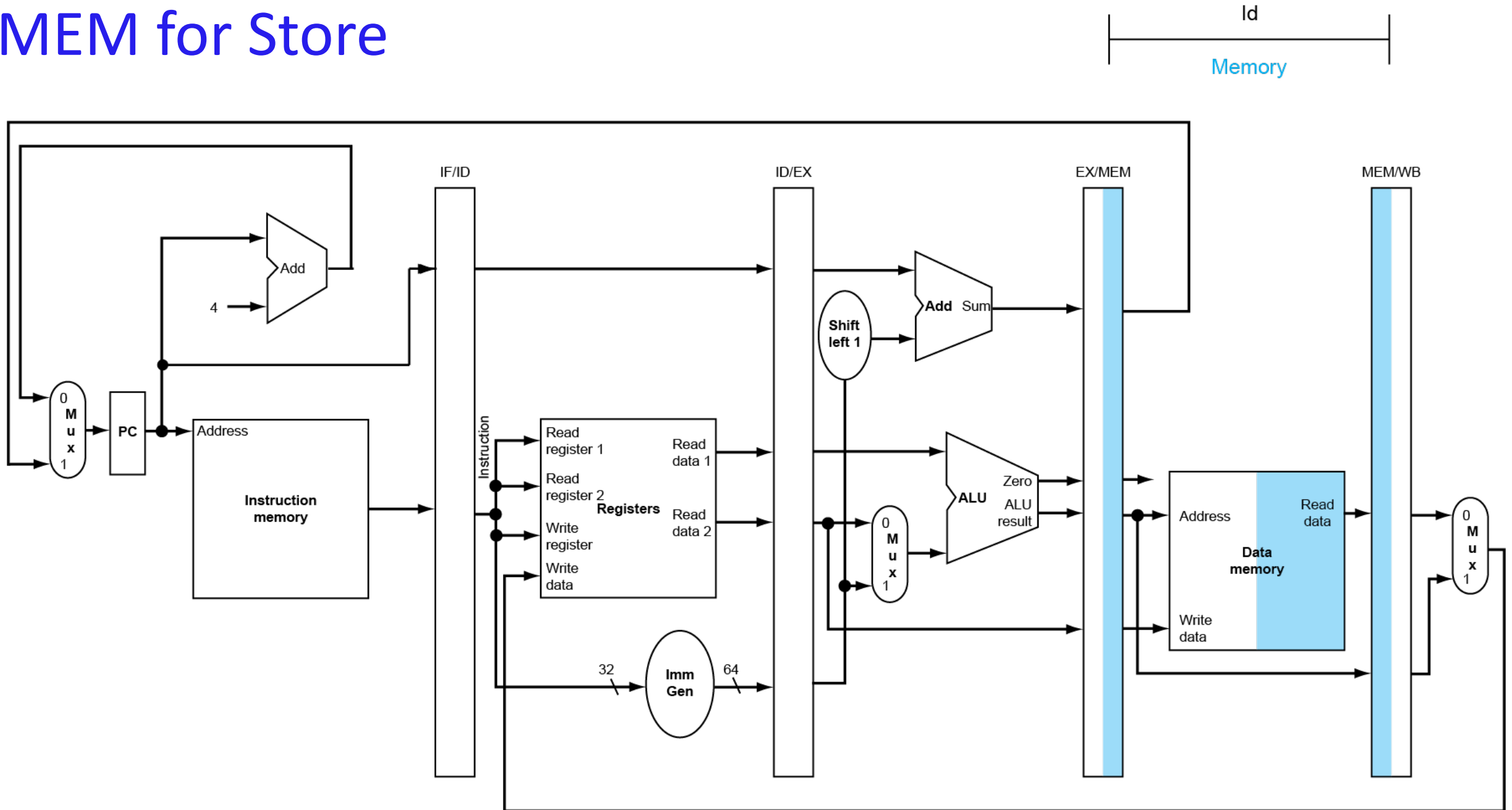



WB for Store

sd
Write-back

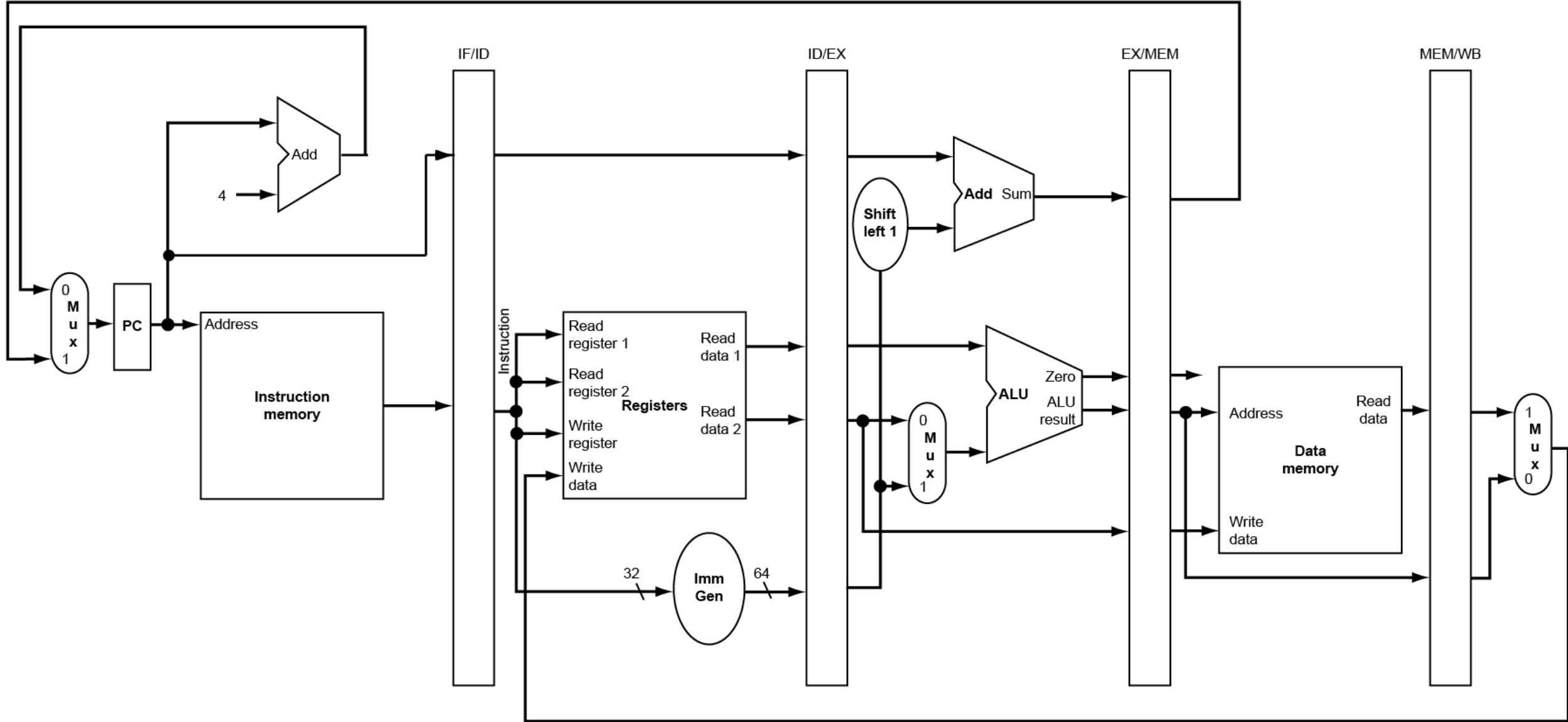


Single-Cycle Pipeline Diagram

- State of pipeline in a given cycle

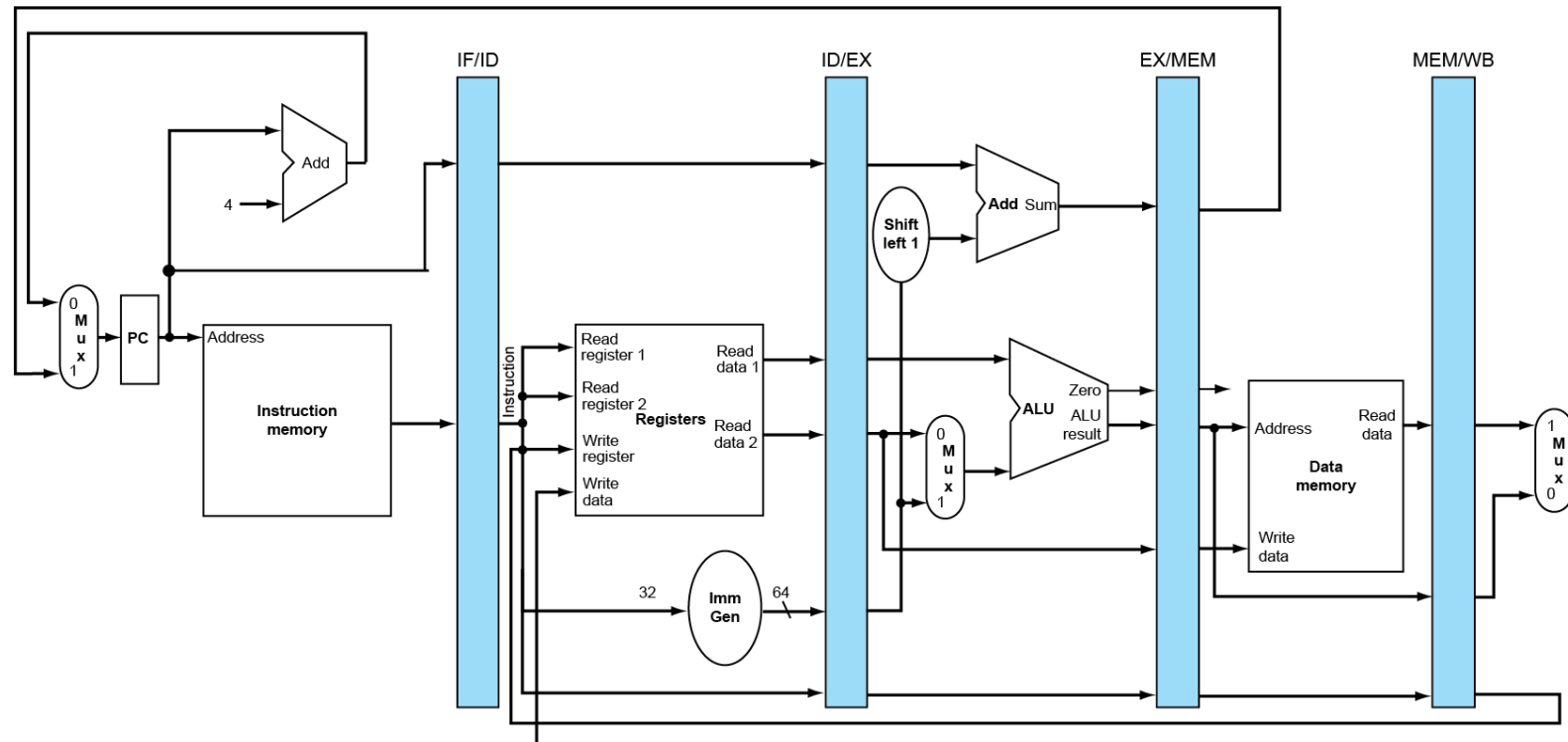 


Multi-Cycle Pipeline Diagram

- Traditional form

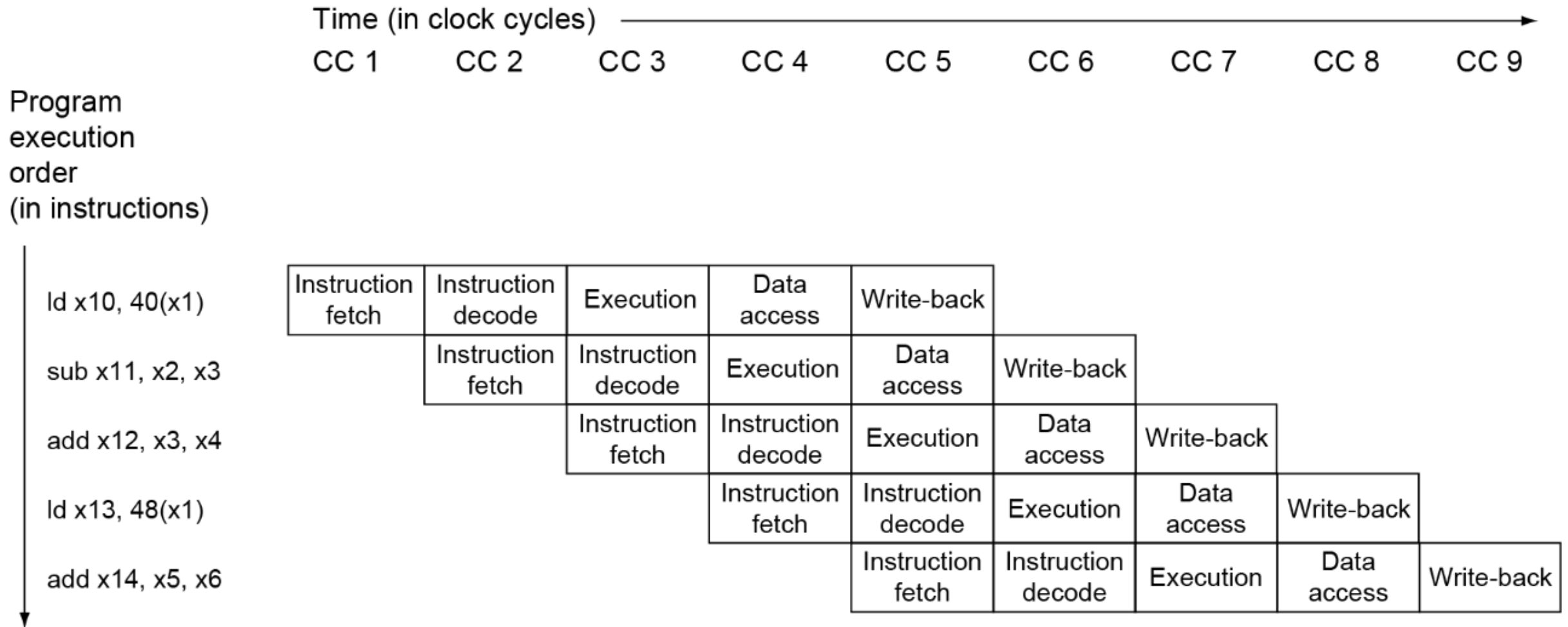

Multi-Cycle Pipeline Diagram

- Form showing resource usage

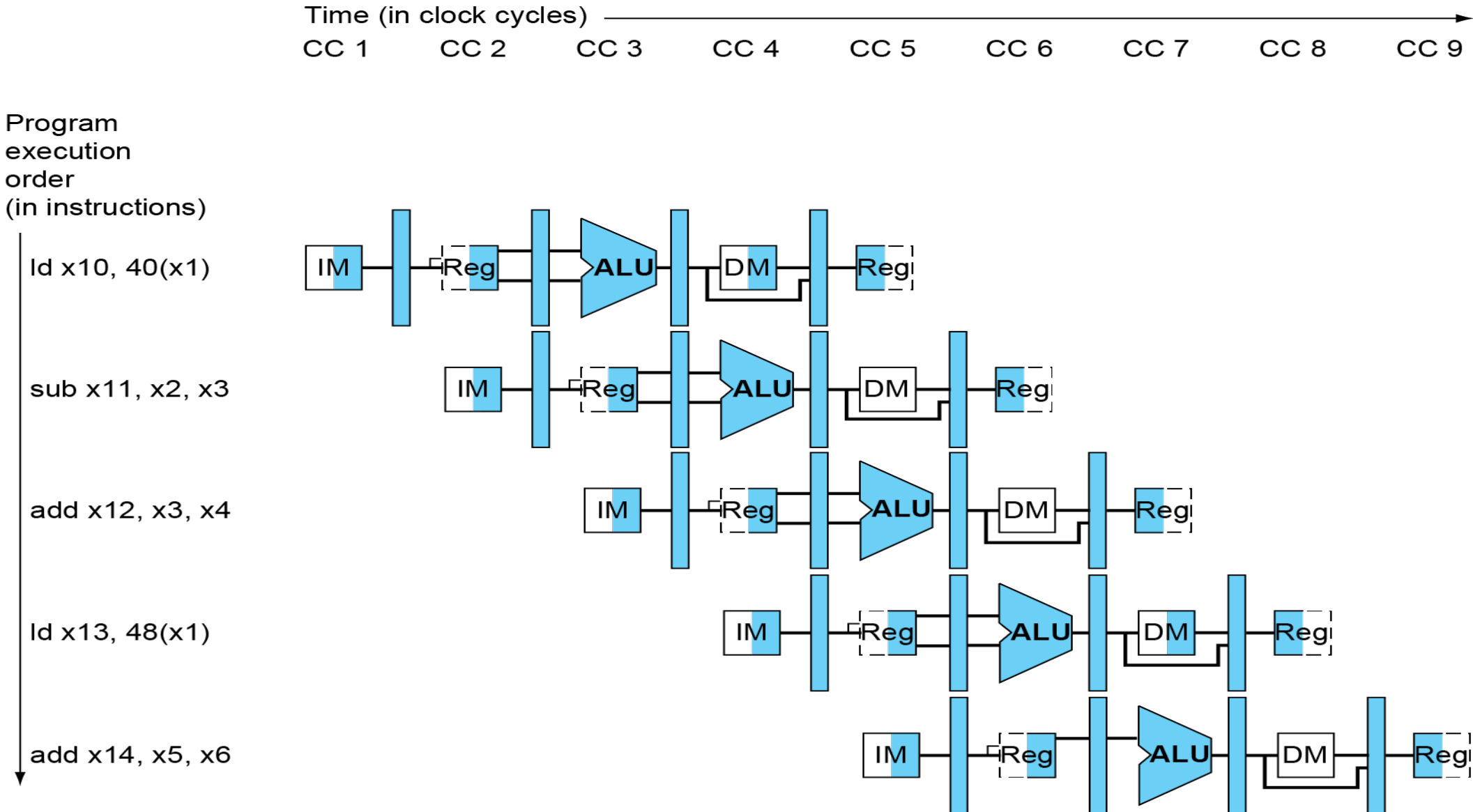

Summary

- Basic single-cycle CPU design
 - Data path vs. control path
 - Clock frequency is limited by the longest delay
- Basic 5-stage pipelined design:
 - Main idea: Parallel processing of different stages of an instruction's execution
 - RISC-V 5-stage pipeline (IF, ID, EXE, MEM, WB)
 - Pipeline hazards: structure, data, control